

**Answers to EEE210 First Midterm AY2018-2019**

1. (a) If  $D_1 \equiv$  forward biased and  $D_2 \equiv$  forward biased then  $V_{out} = V_{in}$  and  $V_{in} > 80$  V. The smallest value of  $V_{in}$  is 80 V.  
(b)  $V_{out} = 80$  V ( $D_1 \equiv$  forward biased and  $D_2 \equiv$  reverse biased).
2. (a)  $V_S = 2.81235$  V  
(b)  $V_S = 2.85$  V
3.  $v_o(0^+) = 0$  V  $\Rightarrow V_D(0^+) = -2$  V  $\Rightarrow D$  is initially reverse biased.  $D$  switches to forward biased at time  $t_p = 24$  ms. Finally:

$$v_o(t) = \begin{cases} 5 - 5 e^{-t/(47 \text{ ms})} \text{ V} & \text{if } 0 \leq t \leq t_p \\ 2 \text{ V} & \text{if } t_p \leq t \end{cases}$$

4. (a)  $43.97 \text{ mA} < I_R(t) < 58.68 \text{ mA}$ .  
(b)  $R_L \geq 116 \Omega$ .