

**Answers to EEE210 final exam AY2013-2014**

1. (a) **Figure (a)**  $I = 0.86 \text{ mA}$ ,  $V = 0 \text{ V}$  (with ideal diodes we would find  $I = 1.0 \text{ mA}$ ,  $V = 0 \text{ V}$ ).

**Figure (b)**  $I = 0 \text{ mA}$ ,  $V = -3.5667 \text{ V}$  (with ideal diodes we would find  $I = 0 \text{ mA}$ ,  $V = -3.3333 \text{ V}$ ).

- (b)  $V_D(0^+) = -12 \text{ V} \Rightarrow D$  is initially reverse biased.  $D$  switches to forward biased at time  $t_p = 13.8629 \text{ ms}$ . Finally:

$$V_o(t) = \begin{cases} 12 - 24e^{-t/(20 \text{ ms})} \text{ V} & \text{if } t \leq t_p = 13.8629 \text{ ms} \\ 0 \text{ V} & \text{if } t \geq t_p = 13.8629 \text{ ms} \end{cases}$$

(c) Refer to course notes.

2. (a)  $V_t = 1 \text{ V}$ ,  $K = 1 \text{ mA/V}^2$ .  
 (b) Set all DC sources to 0, replace all capacitors by short-circuits, replace the MOSFET by its small signal AC model and redraw:

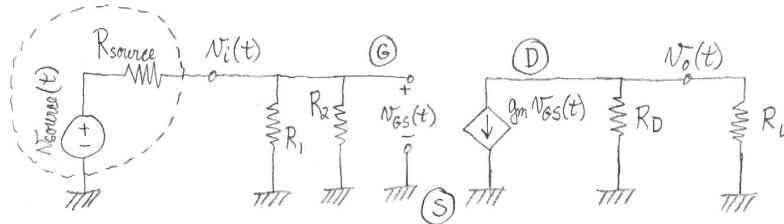


Figure 1:

Voltage gain expression is easily obtained; refer to course notes. We require  $R_D = 1 \text{ k}\Omega$ ,  $g_m = 4 \text{ mS}$ .

- (c) Set all DC sources to 0, replace all capacitors (except  $C_S$ ) by short-circuits, replace the MOSFET by its small signal AC model and redraw:

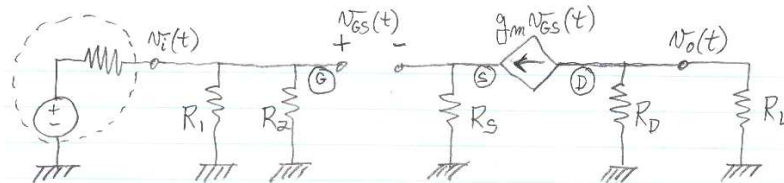


Figure 2:

Voltage gain expression is easily obtained; refer to course notes. We require  $R_S = 500 \Omega$ .

- (d)  $R_1 = R_2 = 24 \text{ M}\Omega$ .
3. (a) Easy. Refer to notes.
- (b) Set all DC sources to 0, replace all capacitors by short-circuits, replace the BJT by its small signal AC model with:

$$h_{ie} = 240.55 \Omega$$

$$h_{fe} = 99$$

and redraw. Easy. Refer to notes.

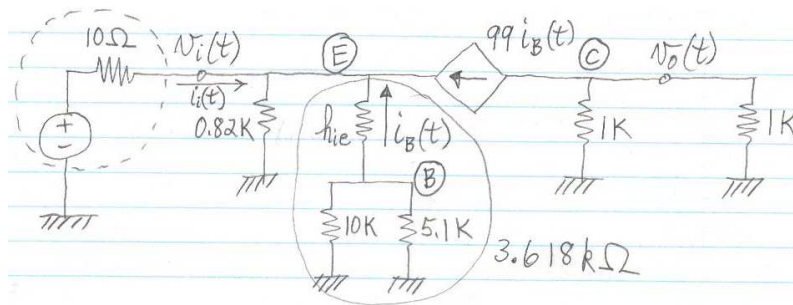


Figure 3:

- (c) Easy. Refer to notes.
- (d)  $Z_{in} = 34.651 \Omega$ ,  $Z_{out} = 1 \text{ k}\Omega$ .
- (e)  $A_I = 0.47409$ ,  $A_P = 6.4866$ .
- (f)  $-0.382 \text{ V} < v_{in}(t) < 0.379 \text{ V}$ .
4. (a)  $OUT = \overline{(A \wedge B)} \vee C$  (also sometimes written as  $OUT = \overline{AB + C}$ ).  
Truth table is easily obtained.
- (b)  $NM_H = NM_L = 1.8 \text{ V}$ .
- (c)  $t_{pHL} = 2.5 \text{ ns}$ .