

Answers to EEE210 final exam AY2014-2015

1. (a)

$$V_{out} = \begin{cases} 40 \text{ V} & \text{if } V_{in} < 40 \text{ V} & (D_1 \equiv \text{off and } D_2 \equiv \text{on}) \\ V_{in} & \text{if } 40 \text{ V} < V_{in} < 80 \text{ V} & (D_1 \equiv \text{on and } D_2 \equiv \text{on}) \\ 80 \text{ V} & \text{if } V_{in} > 80 \text{ V} & (D_1 \equiv \text{on and } D_2 \equiv \text{off}) \end{cases}$$

(b) $V_D(0^+) = -2 \text{ V} \Rightarrow D$ is initially *reverse biased*. D switches to *forward biased* at time $t_0 = 26.05 \text{ ms}$. Finally:

$$v_o(t) = \begin{cases} 4.7 - 4.7 e^{-t/(47 \text{ ms})} \text{ V} & \text{if } t \leq t_0 = 26.05 \text{ ms} \\ 2 \text{ V} & \text{if } t \geq t_0 = 26.05 \text{ ms} \end{cases}$$

2. (a) $R_1 = 150 \text{ k}\Omega$, $R_2 = 150 \text{ k}\Omega$, $R_S = 0.5 \text{ k}\Omega$, $R_D = 0.5 \text{ k}\Omega$.

(b) $g_m = 10 \text{ mS}$

(c) Set all DC sources to 0, replace all capacitors by short-circuits, replace the MOSFET by its small signal AC model with:

$$g_m = 10 \text{ mS}$$

and redraw.

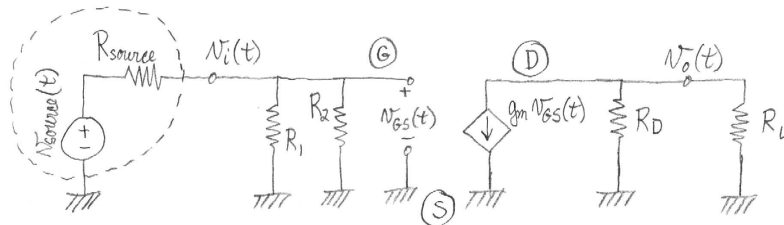


Figure 1:

Voltage gain expression is easily obtained; refer to course notes. We find $A_V = -3.33$.

(d) $Z_{in} = 75 \text{ k}\Omega$.

(e) $Z_{out} = 500 \Omega$.

(f) $R_L = Z_{out} = 500 \Omega$.

3. (a) $R_E \triangleq R_{E1} + R_{E2} = 1.1589 \text{ k}\Omega$, $R_C = 3.5 \text{ k}\Omega$.

(b) $R_1 = 104.35 \text{ k}\Omega$, $R_2 = 24.742 \text{ k}\Omega$.

(c) Set all DC sources to 0, replace all capacitors by short-circuits, replace the BJT by its small signal AC model and redraw ($h_{ie} \approx 1.5 \text{ k}\Omega$ from the graph).

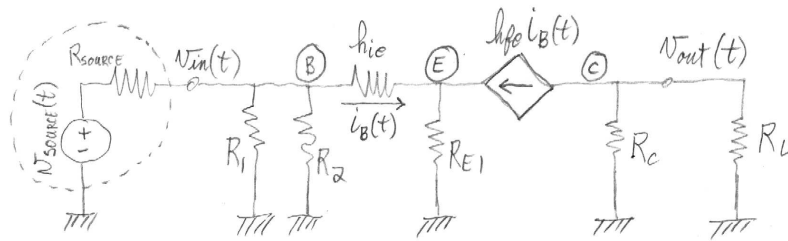


Figure 2:

- (d) Easy; refer to course notes.
- (e) $R_{E1} = 505 \Omega$, $R_{E2} = 654 \Omega$.
- (f) $Z_{in} = 15.88 \text{ k}\Omega$, $Z_{out} = 3.5 \text{ k}\Omega$, $A_P = 39.7$.
- (g) $-1.55 \text{ V} < v_{in}(t) < 1.64 \text{ V}$.
4. (a) Easy.
- (b) i. $t_0 = 4.286 \text{ ns}$
 ii. 3.365 ns
 iii. 7.650 ns
 iv. A.

$$\begin{aligned}
 t_1 &= R_{eq} C \ln(2) \\
 &= 6.93147 \times 10^{-12} R_{eq}
 \end{aligned}$$

B. $R_{eq} = 1.104 \text{ k}\Omega$.