

Answers to EEE210 final exam AY2018-2019

1. (a) **Figure (a)** $I = 0.86 \text{ mA}$, $V = 0 \text{ V}$ (with ideal diodes we would find $I = 1.0 \text{ mA}$, $V = 0 \text{ V}$).
Figure (b) $I = 0 \text{ mA}$, $V = -3.5667 \text{ V}$ (with ideal diodes we would find $I = 0 \text{ mA}$, $V = -3.3333 \text{ V}$).
 (b) $V_D(0^+) = -12 \text{ V} \Rightarrow D$ is initially reverse biased. D switches to forward biased at time $t_p = 13.8629 \text{ ms}$. Finally:

$$V_o(t) = \begin{cases} 12 - 24 e^{-t/(20 \text{ ms})} \text{ V} & \text{if } t \leq t_p = 13.8629 \text{ ms} \\ 0 \text{ V} & \text{if } t \geq t_p = 13.8629 \text{ ms} \end{cases}$$

- (c) Refer to course notes.
2. (a) $V_t = 1 \text{ V}$, $K = 1 \text{ mA/V}^2$.
 (b) Set all DC sources to 0, replace all capacitors by short-circuits, replace the MOSFET by its small signal AC model and redraw:

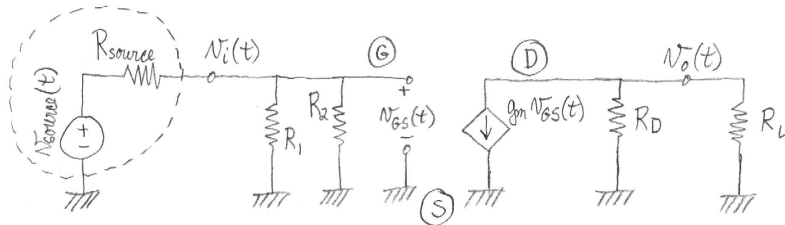


Figure 1:

Voltage gain expression is easily obtained; refer to course notes. We require $R_D = 1 \text{ k}\Omega$, $g_m = 4 \text{ mS}$.

- (c) Set all DC sources to 0, replace all capacitors (except C_S) by short-circuits, replace the MOSFET by its small signal AC model and redraw:

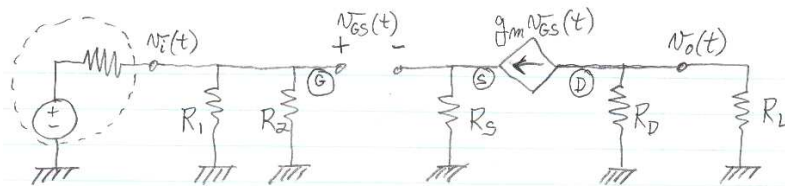


Figure 2:

Voltage gain expression is easily obtained; refer to course notes. We require $R_S = 500 \Omega$.

- (d) $R_1 = R_2 = 24 \text{ M}\Omega$.
3. (a) Easy. Refer to notes.
- (b) Set all DC sources to 0, replace all capacitors by short-circuits, replace the BJT by its small signal AC model with:

$$h_{ie} = 240.55 \Omega$$

$$h_{fe} = 99$$

and redraw. Easy. Refer to notes.


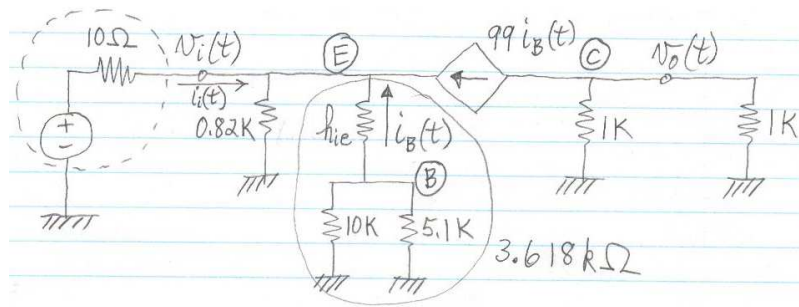


Figure 3:

- (c) Easy. Refer to notes.
- (d) $Z_{in} = 34.651 \Omega$, $Z_{out} = 1 \text{ k}\Omega$.
- (e) $A_V = 0.47409$, $A_P = 6.4866$.
- (f) $-0.382 \text{ V} < v_{in}(t) < 0.379 \text{ V}$.

4. (a)

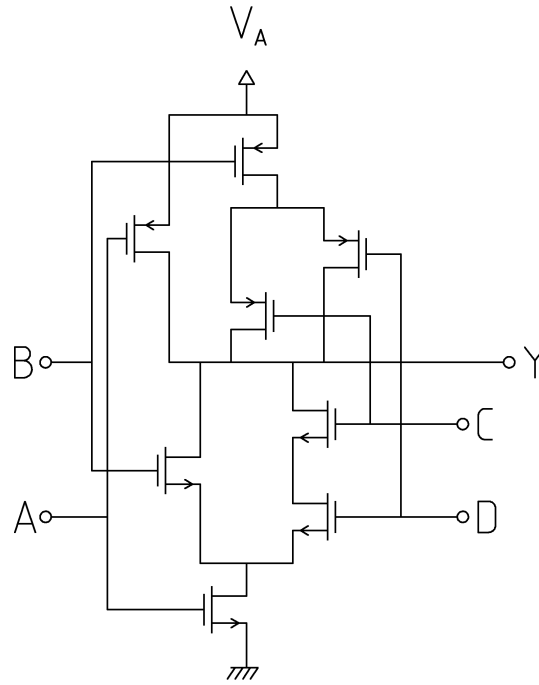

- (b) i. $t_0 = 4.286 \text{ ns}$
 ii. 3.365 ns
 iii. 7.650 ns
 iv. A.

$$t_1 = R_{eq} C \ln(2)$$

$$= 6.93147 \times 10^{-12} R_{eq}$$

B. $R_{eq} = 1.104 \text{ k}\Omega$.