

Repeat twice with a low  $\beta$  and a high  $\beta$ :

$$\text{Low } \beta = \frac{2 \text{ LSD of college\#}}{5} + 75$$

$$\text{High } \beta = \text{Low } \beta + 150$$

EEE210 : Electronic Circuits and Devices

### Lab #7 : Biasing of a BJT

**Experimental work :** Use the NPN transistor 2N3904 or an equivalent. The pin out of the 2N3904 is presented in figure 1.

Build each of the circuits in figure 2. Measure  $V_B$ ,  $V_C$  and  $V_E$ . Calculate  $V_{BE}$ ,  $V_{CE}$ . Calculate  $I_B$ ,  $I_C$  noting that: *using Falstad circuit simulator.*

$$I_B = \frac{15 \text{ V}}{R_1} - \frac{V_B}{R_1 || R_2} \quad (\text{for circuits \#2, \#3, \#4})$$

$$I_C = \frac{15 \text{ V} - V_C}{R_C}$$

*Measure  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_{BE}$ .*

**Note :** Because the base current maybe very small, the above formula for  $I_B$  may yield negative values; this is due to the inaccuracy of the instruments and the resistors.


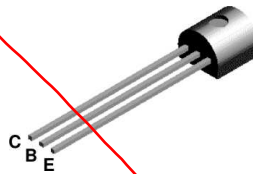



FIGURE 1-

**Report :** Calculate (theoretically) the  $Q$ -point of the BJTs in the circuits of figure 2 using the static current gain  $\beta = 100$ . Compare the theoretical  $Q$ -points with the measured  $Q$ -points.

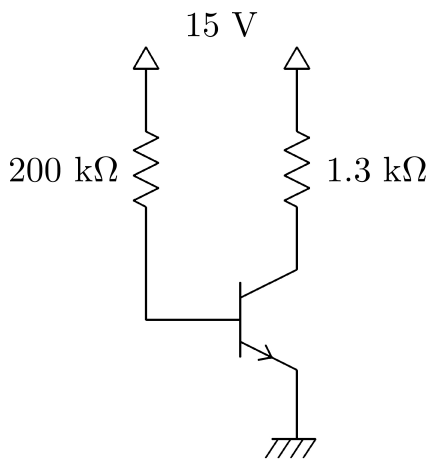
*with low  $\beta$  and  
with high  $\beta$ .*



(a) circuit #1

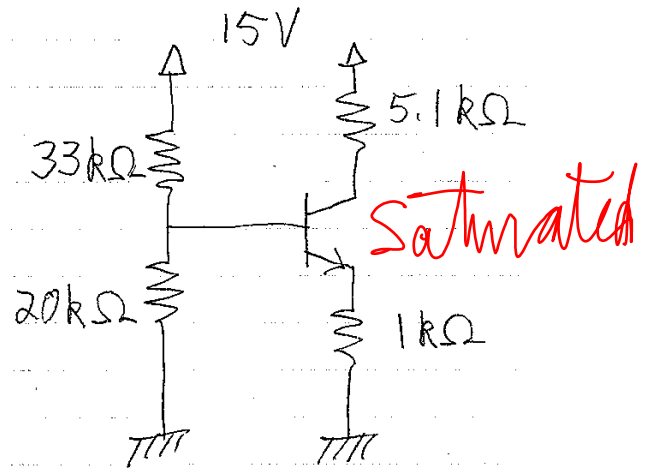


(b) circuit #2

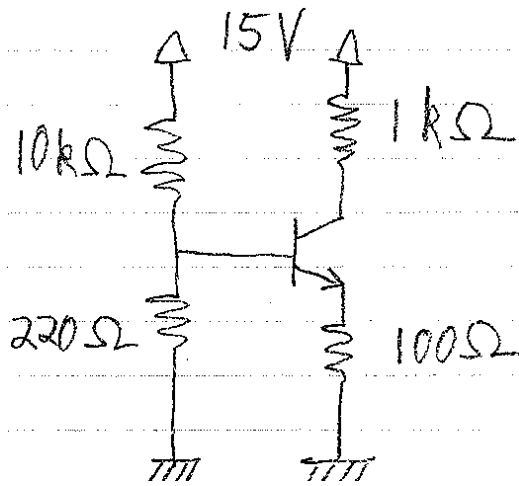

(c) circuit #3

*R.O.*

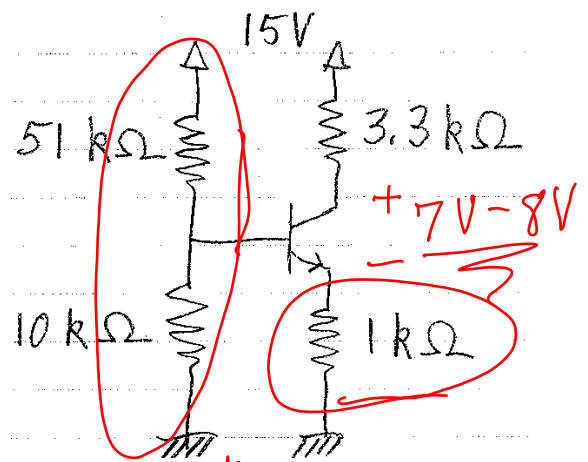

(d) circuit #4

FIGURE 2 -