

## EEE210: Electronic Circuits and Devices

### Lab #6: Common source with unbypassed source resistor amplifier

**Experimental work:** Use the N-channel enhancement type MOSFET 2N7000 or an equivalent. The pin out of the 2N7000 is presented in figure 1.



Figure 1:

1. Build the circuit of figure 2. Measure  $V_{GS}$  and  $V_{DS}$  using a DC voltmeter. Calculate  $I_D$  from those noting that:

$$I_D = \frac{V_{DD} - V_{DS}}{R_S + R_D}$$

where  $V_{DD} = 20$  V,  $R_S = 440$   $\Omega$  and  $R_D = 1.5$  k $\Omega$ . Before going any further, make sure that the MOSFET is biased in the active region.

2. Build the circuit of figure 3. Notice that you only have to add a few components to the circuit of figure 2. Adjust the function generator for  $v_i(t)$  to be a 0-DC sinewave of frequency 1 kHz and peak-peak voltage of 1 V.

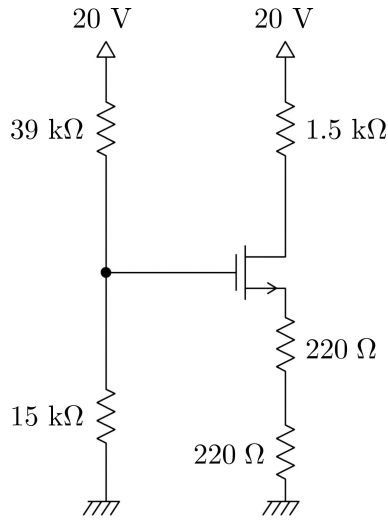


Figure 2:

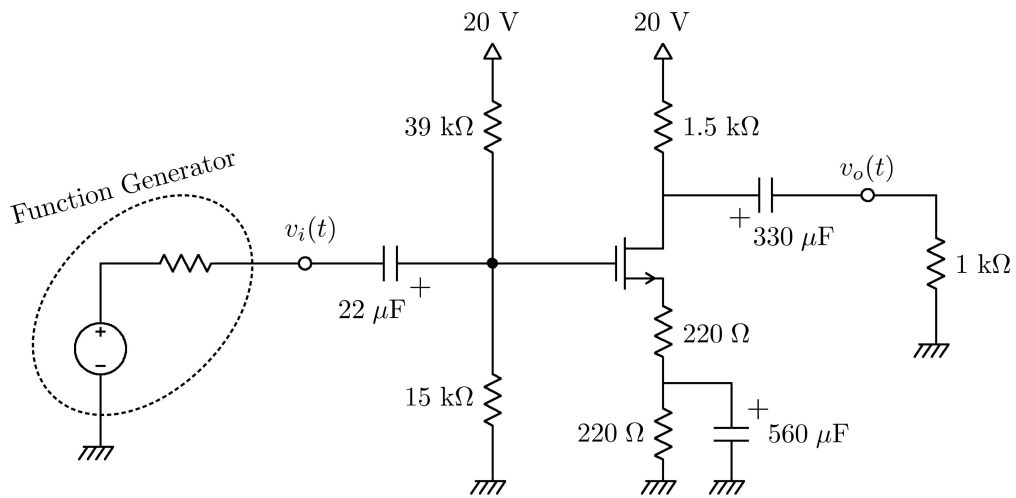


Figure 3:

3. Measure voltage gain

$$A_V = \frac{\text{peak-peak of } v_o(t)}{\text{peak-peak of } v_i(t)}$$

using the oscilloscope.

4. Build the circuit of figure 4 for the measurement of the output impedance  $Z_{out}$ . First set  $R_L = \infty$  and measure the voltage gain

$$A_{V\infty} = \frac{\text{peak-peak of } v_o(t)}{\text{peak-peak of } v_i(t)} \Big|_{R_L=\infty}.$$

Slowly decrease  $R_L$  until the voltage gain drops to  $A_{V\infty}/2$ ; the value of  $R_L$  is then equal to  $Z_{out}$ .

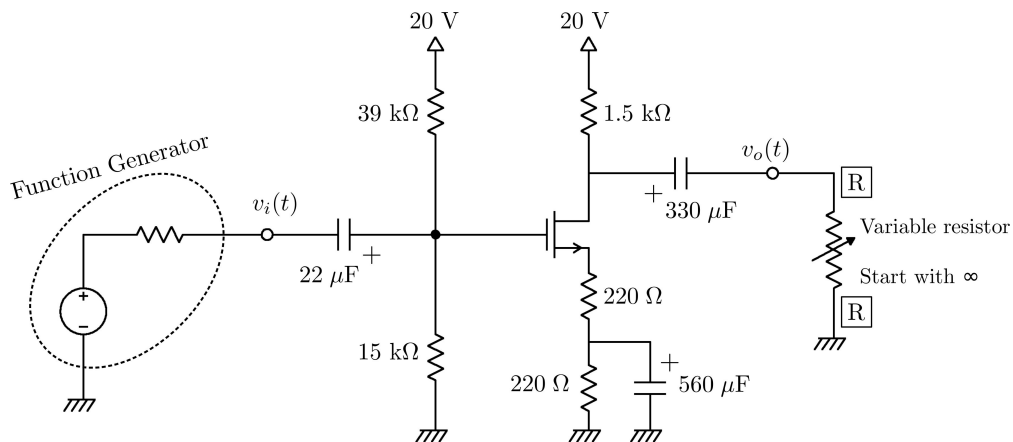


Figure 4:

5. Build the circuit of figure 5 for the measurement of the input impedance  $Z_{in}$ . First set  $R_X = 0$  and measure  $v_i(t)$  and  $v_X(t)$  using the oscilloscope; you should have  $v_X(t) = v_i(t)$ . Slowly increase  $R_X$  until  $v_X(t) = v_i(t)/2$ ; the value of  $R_X$  is then equal to  $Z_{in}$ .

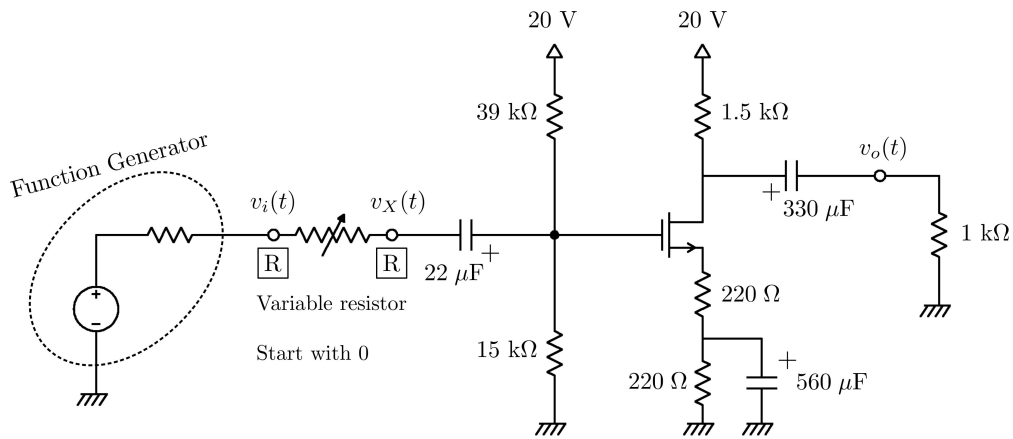


Figure 5:

**Report:**

1. Using  $K = 48 \text{ mA/V}^2$  and  $V_t = 2.1 \text{ V}$ , calculate the Q-point of the MOSFET in the circuit of figure 3 and compare to the measured Q-point.
2. Calculate the voltage gain, the input impedance and the output impedance of the amplifier of figure 3. Compare to the measured values.