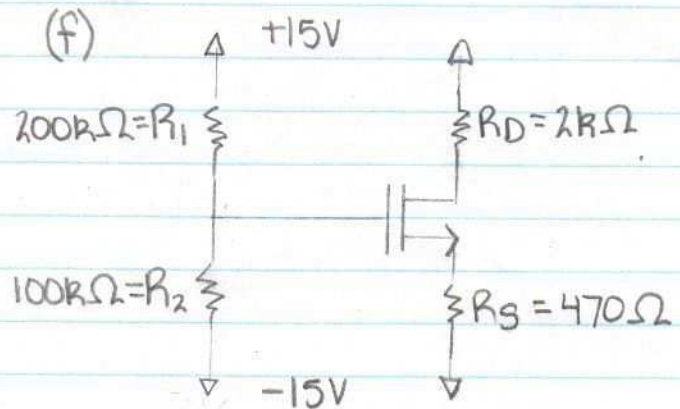
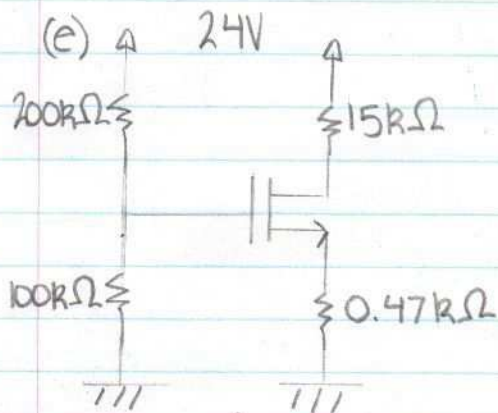
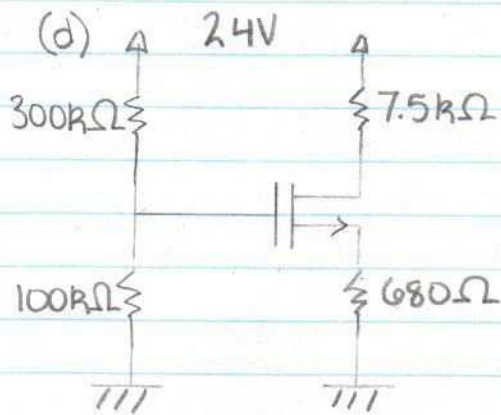
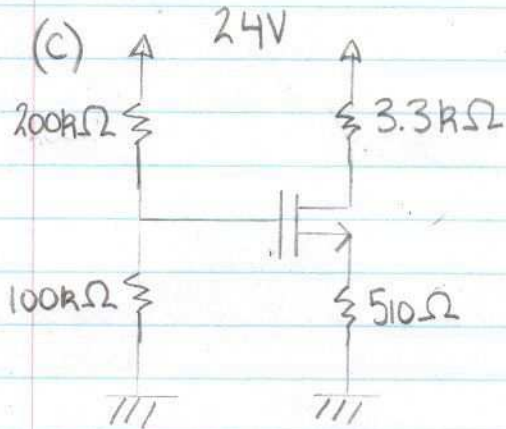
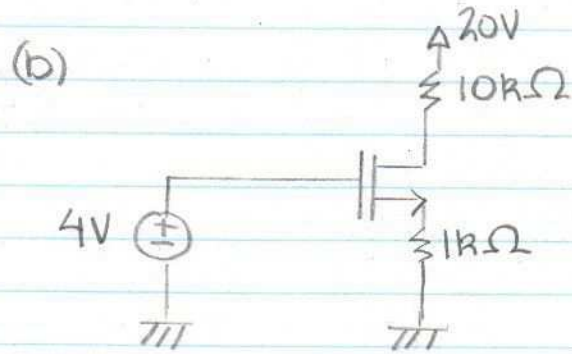
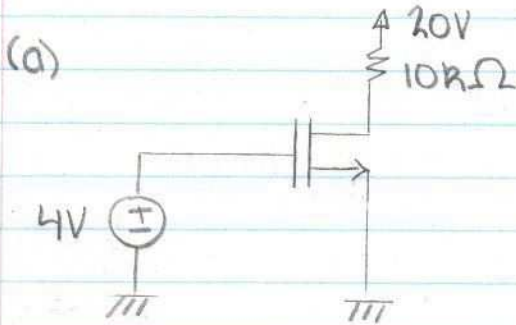


Problem: The parameters of the MOSFETs in the circuits below are $K=0.2\text{ mA/V}^2$ and $V_t=1.5\text{ V}$. Calculate the Q-points of the MOSFETs.



Answers:

(a) $V_{GS} = 4V$

$I_D = 1.25mA$

$V_{DS} = 7.5V$

active

(b) $V_{GS} = 3.33V$

$I_D = 0.669873mA$

$V_{DS} = 12.6314V$

active

(c) $V_{GS} = 5.9658V$

$I_D = 3.9887mA$

$V_{DS} = 8.803V$

active

(d) $V_{GS} = 4.65V$

$I_D = 1.985mA$

$V_{DS} = 7.7638V$

active

(e) $V_{GS} = 7.292V$

$I_D = 1.507mA$

$V_{DS} = 0.692V$

ohmic

(f) $V_{GS} = 7.0767V$

$I_D = 6.220mA$

$V_{DS} = 14.637V$

active