
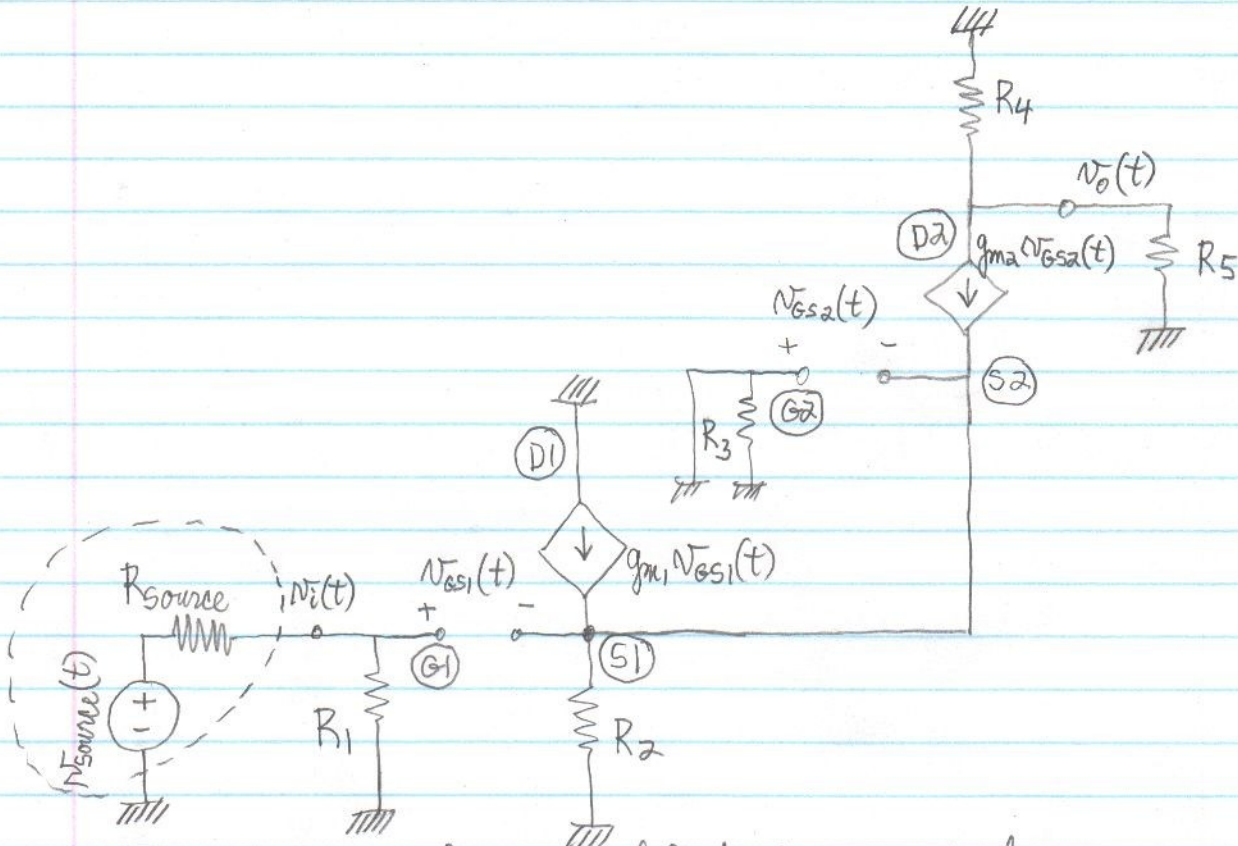


Solution #1

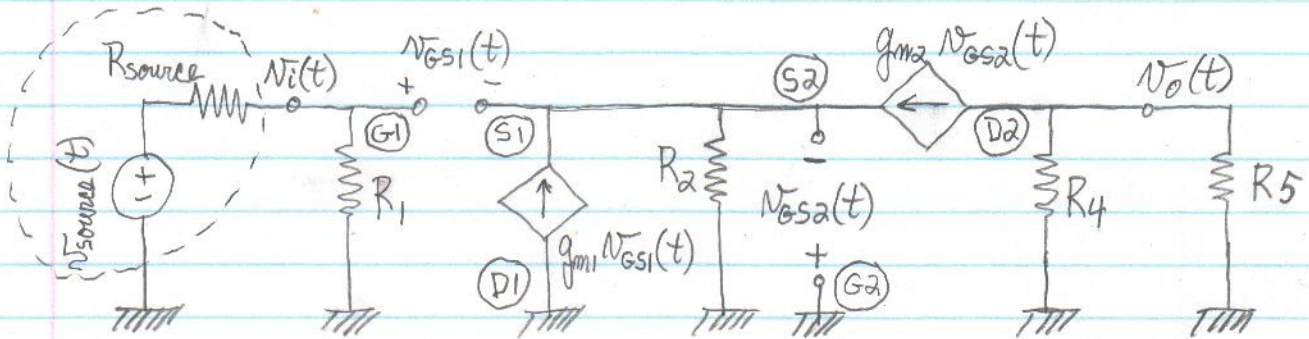We draw the circuit with the DC sources set to 0, the capacitors replaced by short-circuits, and the MOSFETs replaced by their small signal AC model:




Redrawn in the simplified form, it becomes:



Solution #2

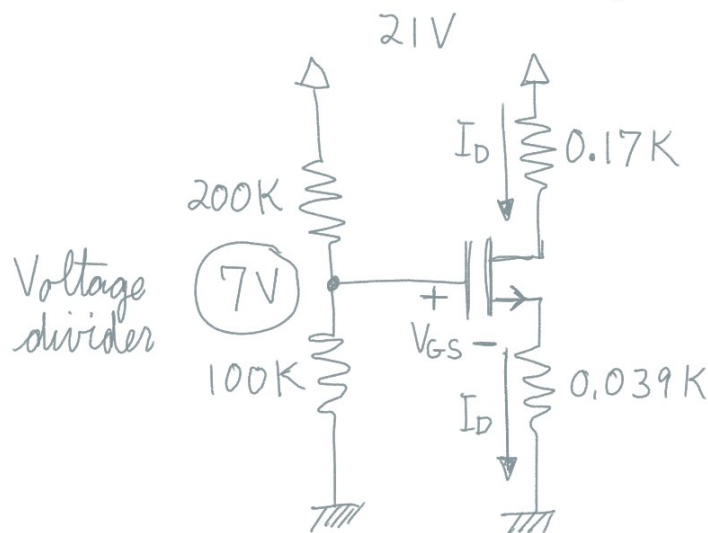(a) First assume, as suggested that the MOSFET is biased in the active region:



The equations are

$$I_D = 48 (V_{GS} - 2.1)^2 \quad (1)$$

$$V_{GS} = 7 - 0.039 I_D \quad (2)$$

and by substituting (2) in (1) we obtain

$$\begin{aligned} I_D &= 48 (4.9 - 0.039 I_D)^2 \\ &= 48 (4.9^2 - 2 \times 4.9 \times 0.039 I_D + 0.039^2 I_D^2) \\ &= 1152.48 - 18.3456 I_D + 0.073008 I_D^2 \end{aligned}$$

The solutions are:

$$\begin{cases} I_D = 90.444 \text{ mA} \Rightarrow V_{GS} = 3.4727 \text{ V} \\ I_D = 174.535 \text{ mA} \Rightarrow V_{GS} = 0.19314 \text{ V} \end{cases}$$

eliminate cuz less than $V_t = 2.1 \text{ V}$

With $I_D = 90.444 \text{ mA}$ we then obtain

$$\begin{aligned} V_{DS} &= 21 - 0.17 I_D - 0.039 I_D \\ &= 2.097 \text{ V} \end{aligned}$$

which is larger than $V_{GS} - V_t = 1.3727 \text{ V}$ and the MOSFET is consequently biased in the active region as assumed.

(b) With same R_1 , R_2 and R_S equations (1) and (2) above still hold and if V_{DS} is to become 10 V instead of 2.097 V then the MOSFET is clearly active. R_D is then simply obtained from

$$V_{DS} = 10 = 21 - (R_D + 0.039) \times 90.444$$


$$\Rightarrow R_D = 82.622 \Omega$$



Solution #3

From the Q-point we find $g_m = 2K(V_{GS} - V_t)$
 $= 2 \times 50 \times (2.64 - 2.5)$
 $= 14 \text{ mS}$

The AC model of the circuit is

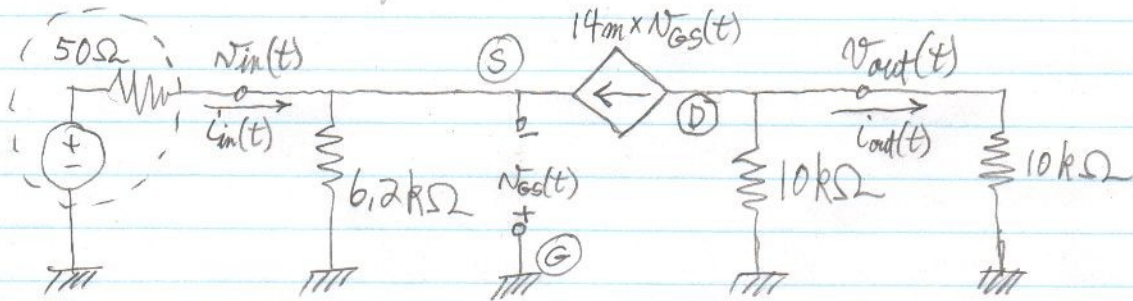

We easily find

$$(i) v_{out}(t) = -v_{GS}(t) \times 14 \text{ mS} \times (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$\uparrow \quad \quad \quad v_{GS}(t) = -v_{in}(t)$$

$$= 70 v_{in}(t) \quad \rightarrow \quad \boxed{A_v = 70}$$

$$(ii) i_{in}(t) = \frac{v_{in}(t)}{6.2 \text{ k}\Omega} - 14 \text{ mS} \times v_{GS}(t)$$

$$\quad \quad \quad \uparrow \quad \quad \quad v_{GS}(t) = -v_{in}(t)$$

$$= \frac{v_{in}(t)}{6.2 \text{ k}\Omega} + \frac{v_{in}(t)}{1/14 \text{ mS}}$$

$$= \frac{v_{in}(t)}{(6.2 \text{ k}\Omega \parallel (1/14 \text{ mS}))} = \frac{v_{in}(t)}{70.6 \Omega} \quad \rightarrow \quad \boxed{Z_{in} = 70.6 \Omega}$$

$$(iii) A_I = \frac{A_v Z_{in}}{R_L} = \frac{70 \times 70.6 \Omega}{10 \text{ k}\Omega} \quad \rightarrow \quad \boxed{A_I = 0.494}$$

$$(iv) A_P = A_v \times A_I \quad \rightarrow \quad \boxed{A_P = 34.59}$$

(v) $Z_{out} = V/I$ in the circuit below:

