

Solution #1:

ψ_p

$$= A \sin(t + \theta)$$

$$\psi_m(t) = A e^{-2t}$$

$$A \cos(t + \theta) + 2A \sin(t + \theta) = \cos(t) \\ + 2A \cos(t + \theta - 90^\circ) = \cos(t)$$

$$A \angle \theta + 2A \angle (\theta - 90^\circ) = 1$$

$$A \angle \theta (1 + (-2j)) = 1$$

$$A \angle \theta = \frac{1}{1 - 2j} = 0.447 \angle 63.435^\circ$$

$$\psi_p(t) = 0.447 \sin(t + 63.435^\circ)$$

$$\psi(t) = A e^{-2t} + 0.447 \sin(t + 63.435^\circ)$$

$$\psi(0) = 0 = A + 0.447 \sin(63.435^\circ)$$

$$\Rightarrow A = -0.447 \sin(63.435^\circ) \\ = -0.39981$$


$$\Rightarrow \psi(t) = 0.447 \sin(t + 63.435^\circ) - 0.39981 e^{-2t}$$

Solution#2:

Voir notes de cours.

Solution #3:

(a) Avec le court-circuit virtuel on a :

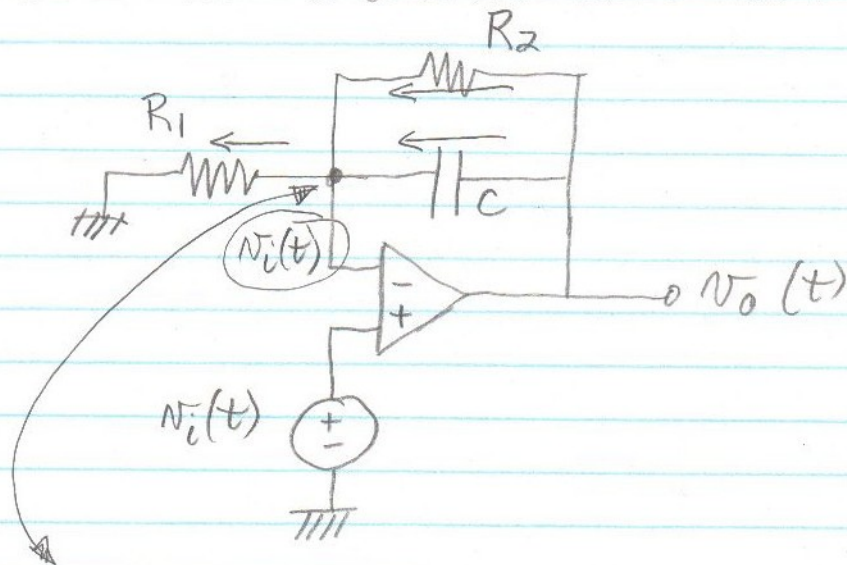

LCK donne :

$$\frac{V_o(t) - V_i(t)}{R_2} + C \frac{d(V_o(t) - V_i(t))}{dt} = \frac{V_i}{R_1}$$

qui est réécrit comme :

$$V_o'(t) + \frac{V_o(t)}{R_2 C} = V_i'(t) + \frac{V_i(t)}{(R_1 \parallel R_2) C}$$

En remplaçant

$$R_1 = R_2 = 5 \Omega$$

$$C = 0.15 F$$

on obtient

$$V_o'(t) + 4/3 V_o(t) = V_i'(t) + 8/3 V_i(t)$$