

## Tutorial #7

### Solutions

P5.7 a) in DC, the impedance of the inductor is 0 and the impedance of the capacitor is infinite, so circuit is simply equivalent to resistor  $R = 3 \text{ k}\Omega$

b) here  $\omega = 5000 \text{ rad/s}$

$$\text{so } Z_L = j5000 \times 1 = j5000 \Omega$$

$$Z_C = -\frac{j}{5000 \times 2.5 \times 10^{-7}} = -j800 \Omega$$

$$\text{and } Z = \frac{Z_C (R + Z_L)}{R + Z_L + Z_C} = \frac{-j800 \times (3000 + j5000)}{3000 + j4200}$$

$$= 904 \angle -85.5^\circ \quad (\text{erreur dans le livre})$$


$$\text{P5.11- a) } 3 + j4 = 5 \angle 53^\circ$$

$$\text{so } i(t) = 5\sqrt{2} \cos(\omega t + 53^\circ)$$

$$\text{b) } v(t) = 3\sqrt{2} \cos(\omega t - \pi/4)$$

$$\text{c) } i(t) = 4\sqrt{2} \cos(\omega t - 90^\circ)$$

P5.17

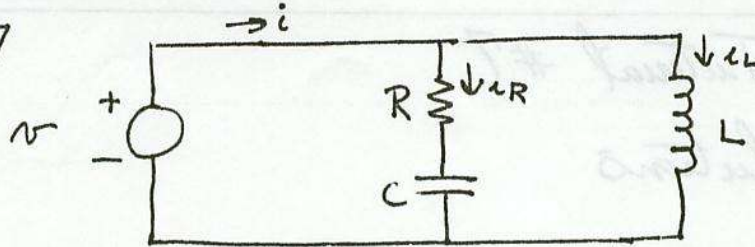


$$R = 2 \Omega$$

$$L = 0,3 \text{ H}$$

$$i_R = 10\sqrt{2} \cos(10t + 45^\circ)$$

$$Z_L = j 10 \times 0,3 = j3 \Omega$$

a) and b)

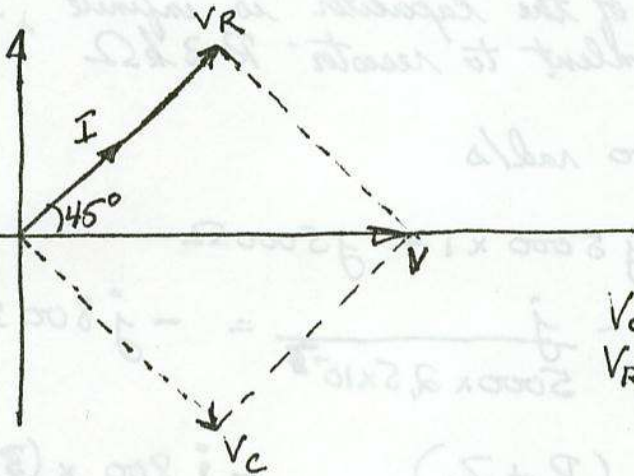


$v_C$  has a magnitude equal to  $v_R$  and a phase of  $-45^\circ$ .

c) from the phasor diagram

$$\begin{aligned} \underline{V} &= \underline{V}_R + \underline{V}_C = 2 \Omega \times 10 \angle 45^\circ + \underline{V}_C \\ &= 20 \angle 45^\circ + 20 \angle -45^\circ \\ &= \cancel{20\sqrt{2}} \ 20\sqrt{2} \angle 0^\circ \end{aligned}$$

$$\text{so } v(t) = 40 \cos 10t$$

P5.24

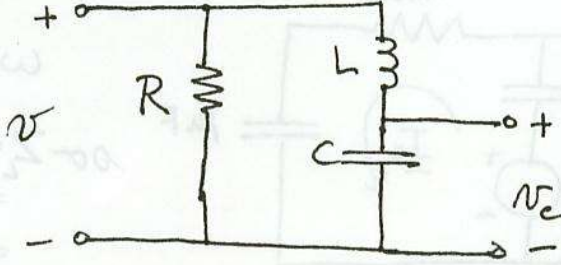

$$v = 5\sqrt{2} \cos 5t$$

$$R = 2\Omega$$

$$L = 1H, Z_L = j5 \times 1 = j5\Omega$$

$$C = 0,06F, Z_C = \frac{-j}{5 \times 0,06} = -j3,33\Omega$$

a) admittance of branch made of  $R$ :  $\frac{1}{R} = \frac{1}{2} \sigma$

admittance of branch made of  $L$  and  $Z$

$Z$  for that branch is:  $Z_{L-C} = j5 - j3,33 = j1,66\Omega$

so  $Y$  is

$$Y_{L-C} = \frac{1}{j1,66} = -j\frac{3}{5} \sigma$$


and admittance of total system is

$$Y = (0,5 - j0,6) \sigma$$


b)  $\underline{I}_R = \frac{V}{2\Omega} = 2,5 \angle 0^\circ$

$$\underline{I}_L = Y_{L-C} V = -j0,6 \times 5 \angle 0^\circ = 3 \angle -90^\circ$$

$$\underline{I} = 2,5 - j3$$

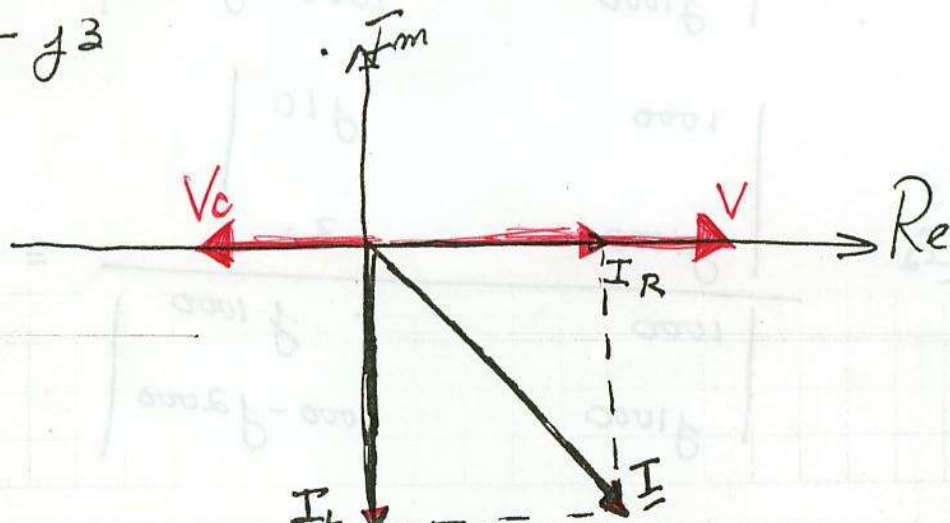

AP5-5.

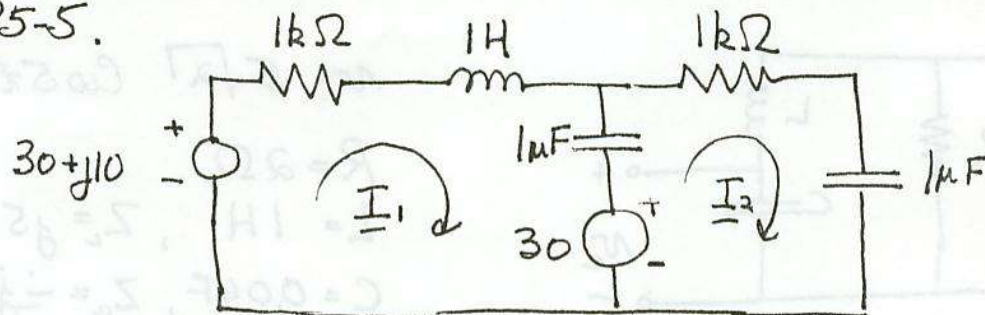

$$\omega = 1000 \text{ rad/s}$$

$$\begin{aligned} \text{so } Z_L &= j\omega L \\ &= j1000 \times 1 \\ &= j1000 \Omega \end{aligned}$$

$$\begin{aligned} \text{and } Z_C &= \frac{-j}{\omega C} = \frac{-j}{1000 \times 10^{-6}} \\ &= -j1000 \end{aligned}$$

a) so loop equations will be

$$\begin{bmatrix} 1000 & j1000 \\ j1000 & 1000 - j2000 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} j10 \\ 30 \end{bmatrix}$$

$$\text{so } \underline{I}_1 = \frac{\begin{vmatrix} j10 & j1000 \\ 30 & 1000 - j2000 \end{vmatrix}}{\begin{vmatrix} 1000 & j1000 \\ j1000 & 1000 - j2000 \end{vmatrix}} = 0,01 \angle 40^\circ$$

and

$$\underline{I}_2 = \frac{\begin{vmatrix} 1000 & j10 \\ j1000 & 30 \end{vmatrix}}{\begin{vmatrix} 1000 & j1000 \\ j1000 & 1000 - j2000 \end{vmatrix}} = 0,01\sqrt{2} \angle 45^\circ$$

A) Node equation will be (There is a single node)

$$\frac{V_b - (30 + j10)}{1000 + j1000} + \frac{V_b - 30}{-j1000} + \frac{V_b}{1000 - j1000} = 0$$


$$\text{So } V_b \left( \frac{1}{1000 + j1000} + \frac{j}{1000} + \frac{1}{1000 - j1000} \right) = \frac{30 + j10}{1000 + j1000} + \frac{30j}{1000}$$

$$\frac{V_b}{1000} \left( \frac{1-j}{2} + j + \frac{1+j}{2} \right) = \left\{ \frac{(30 + j10)(1-j)}{2} + 30j \right\} \times \frac{1}{1000}$$

$$V_b (1 + j) = 20 + 20j = 20(1 + j)$$

$$V_b = 20 \angle 0^\circ$$

APS.11

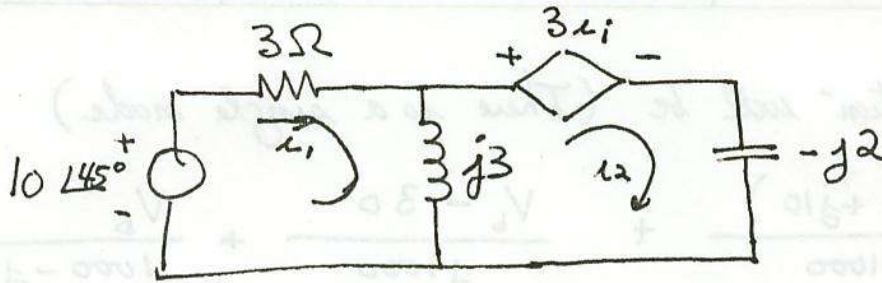

Reactive component impedances have been calculated using  $\omega = 100 \text{ s}^{-1}$

We use mesh method with the 2 currents shown

$$10 \angle 45^\circ - 3 \underline{I}_1 - j3 (\underline{I}_1 - \underline{I}_2) = 0 \quad \text{mesh 1}$$

$$-j3 (\underline{I}_2 - \underline{I}_1) - 3 \underline{I}_1 + j2 \underline{I}_2 = 0 \quad \text{mesh 2}$$

$$\text{or } (3 + j3) \underline{I}_1 - j3 \underline{I}_2 = 10 \angle 45^\circ$$

$$(3 - j3) \underline{I}_1 + j \underline{I}_2 = 0$$

or in matrix form:

$$\begin{bmatrix} 3 + j3 & -j3 \\ 3 - j3 & j \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 45^\circ \\ 0 \end{bmatrix}$$

Then:

$$\underline{I}_1 = \frac{\begin{vmatrix} 10 \angle 45^\circ & -j3 \\ 0 & j \end{vmatrix}}{\begin{vmatrix} 3 + j3 & -j3 \\ 3 - j3 & j \end{vmatrix}} = \frac{10j \angle 45^\circ}{j(3 + j3) + j3(3 - j3)}$$

$$= \frac{10 \angle 135^\circ}{6 + j12} = 0,75 \angle 71,6^\circ \text{ A}$$

$$\text{and } i_1(t) = 0,75 \sqrt{2} \cos(100t + 71,6^\circ) \text{ A}$$